

# **Powering the AM335x, AM437x, and AM438x with TPS65218D0**

This user's guide is a reference for connectivity between the TPS65218D0 power management IC (PMIC) and the AM335x, AM437x, or AM438x processor. For detailed information about the TPS65218D0, AM335x, AM437x, or AM438x, see their respective data sheets.

### **Contents**

1	TPS65218D0 Overview .....	1
2	Connection Diagram for TPS65218D0 and AM335x.....	2
3	Power Rails for TPS65218D0 and AM335x .....	3
4	Connection Diagram for TPS65218D0 and AM437x.....	4
5	Power Rails Connections for TPS65218D0 and AM437x .....	5
6	Connection Diagram for TPS65218D0 and AM438x.....	6
7	Power Rails Connections for TPS65218D0 and AM438x .....	7
8	Power-Up and Power-Down Sequence for TPS65218D0.....	8
9	Memory Voltage Selection.....	9
10	Using LPDDR2 Memory .....	10
11	Warm Reset.....	12
12	Pullup Resistors .....	12

### **List of Figures**

1	Connection Diagram for TPS65218D0 and AM335x.....	2
2	Connection Diagram for TPS65218D0 and AM437x.....	4
3	Connection Diagram for TPS65218D0 and AM438x.....	6
4	TPS65218D0 Sequence Timing Diagram .....	8
5	Connection Diagram for TPS65218D0, AM437x, and LPDDR2 Memory.....	10
6	Connection Diagram for TPS65218D0, AM438x, and LPDDR2 Memory.....	11
7	Warm Reset Functionality .....	12

### **List of Tables**

1	Power Rails for TPS65218D0 and AM335x.....	3
2	Power Rails for TPS65218D0 and AM437x.....	5
3	Power Rails for TPS65218D0 and AM438x.....	7
4	TPS65218D0 Power-Up Sequence .....	8
5	DCDC3 Voltage Selection .....	9

## **Trademarks**

All trademarks are the property of their respective owners.

## **1 TPS65218D0 Overview**

The TPS65218D0 is an optimized and highly integrated power management solution for the AM335x, AM437x, and AM438x processor. Features of the TPS65218D0 include:

- Three DC-DC step-down converters
- One LDO

- Three load switches
- Two micro-power DC-DC step-down converters
- Power path management for battery backup of the processor RTC
- Integrated voltage supervisor

## 2 Connection Diagram for TPS65218D0 and AM335x

The block diagram shown in Figure 1 shows the connections between the TPS65218D0 and the AM335x. Power rails and digital and analog signals are shown. The power rails may be used to power additional parts of the system.

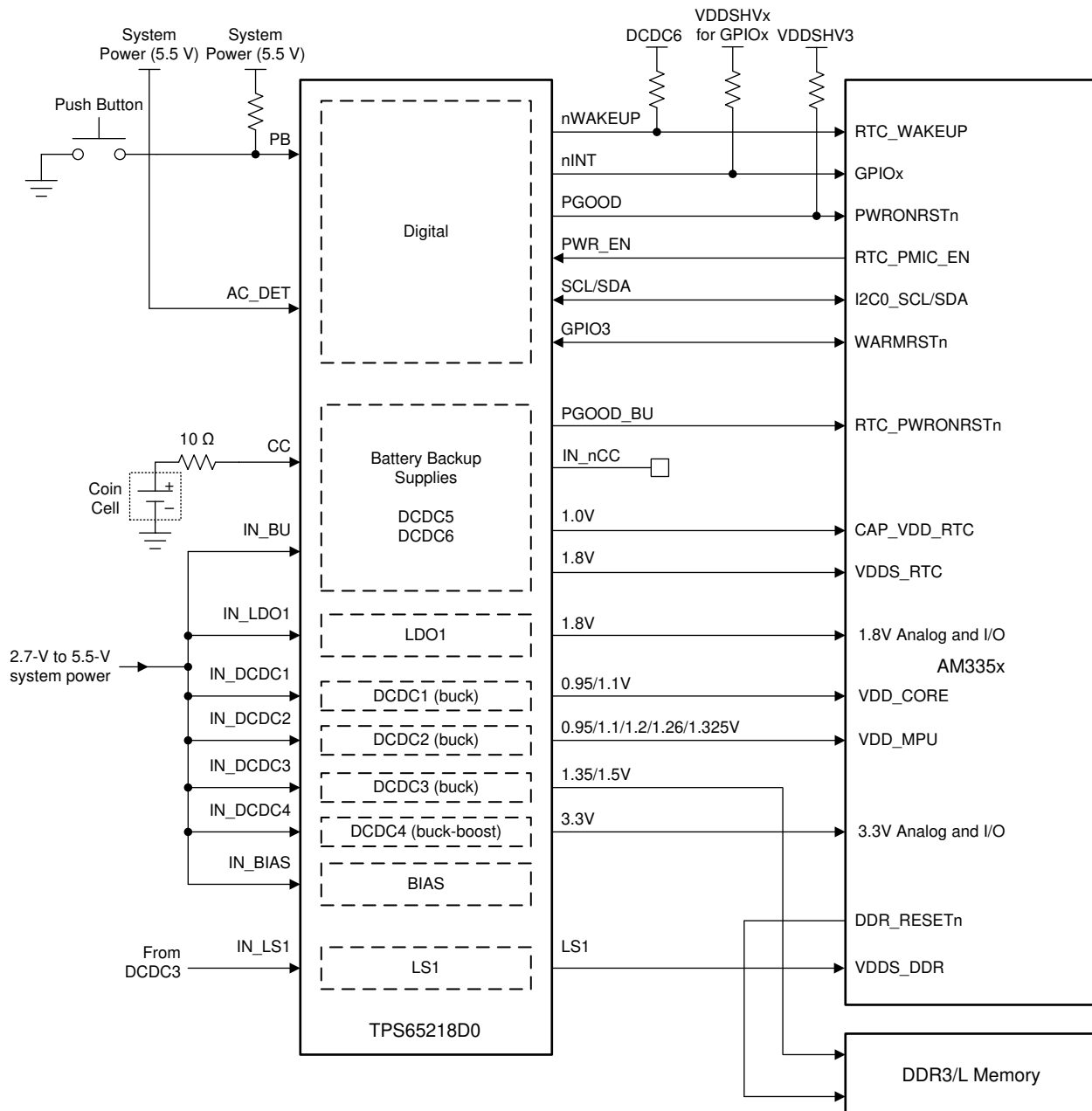


Figure 1. Connection Diagram for TPS65218D0 and AM335x

### 3 Power Rails for TPS65218D0 and AM335x

[Table 1](#) matches the AM335x power terminals with the appropriate power rail from the TPS65218D0.

**Table 1. Power Rails for TPS65218D0 and AM335x**

TPS65218D0	Voltage (V)	AM335x
DCDC1	0.95/1.1	VDD_CORE
DCDC2	0.95/1.1/1.2/1.26/1.325	VDD_MPU
DCDC3	1.35/1.5	DDR3L/DDR3 Memory VDDS_DDR
DCDC4	3.3	VDDSHVx (3.3 V)
		VDDA3P3V_USB0/1
DCDC5	1.0	CAP_VDD_RTC
DCDC6	1.8	VDDS_RTC
LDO1	1.8	VDDS
		VDDSHVx (1.8 V)
		VDDS_SRAM_CORE_BG
		VDDS_SRAM_MPU_BB
		VDDS_PLL_DDR
		VDDS_PLL_CORE_LCD
		VDDS_OSC
		VDDA1P8V_USB0/1
		VDDA_ADC

DCDC3 voltage is initially selected through the choice of resistor on the DC34\_SEL pin. Each output voltage can be changed dynamically while the TPS65218D0 is in active mode. This requires the use of I<sup>2</sup>C commands to the TPS65218D0.

#### 4 Connection Diagram for TPS65218D0 and AM437x

The block diagram shown in Figure 2 shows the connections between the TPS65218D0 and AM437x. Power rails and digital and analog signals are shown. The power rails may be used to power additional parts of the system.

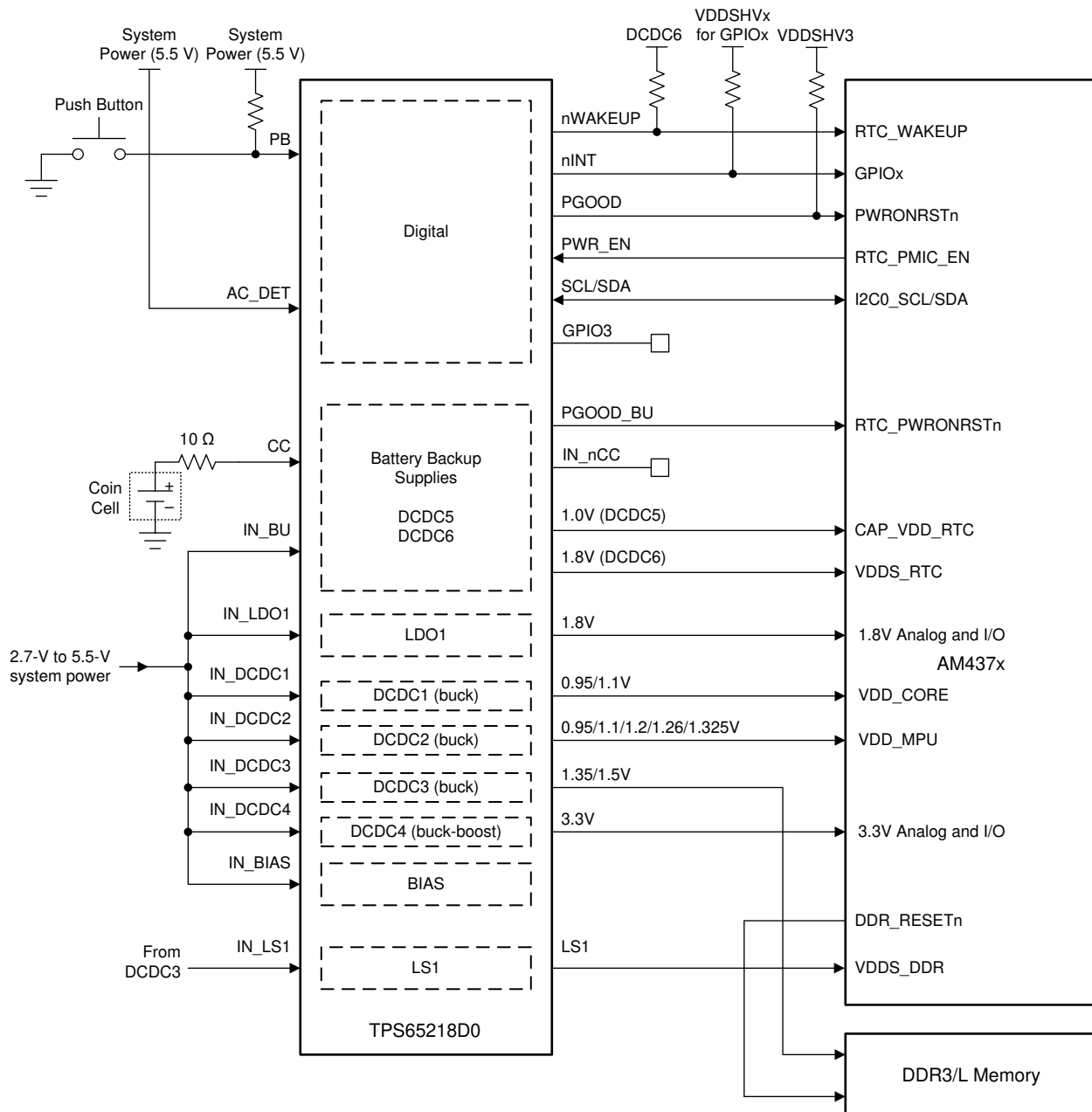


Figure 2. Connection Diagram for TPS65218D0 and AM437x

## 5 Power Rails Connections for TPS65218D0 and AM437x

[Table 2](#) matches the AM437x power terminals with the appropriate power rail from the TPS65218D0.


**Table 2. Power Rails for TPS65218D0 and AM437x**

TPS65218D0	Voltage (V)	AM437x
DCDC1	0.95/1.1	VDD_CORE
DCDC2	0.95/1.1/1.2/1.26/1.325	VDD_MPU
DCDC3	1.2/1.35/1.5	LPDDR2/DDR3L/DDR3 Memory
DCDC4	3.3	VDDSHVx(3.3 V)
		VDDA3P3V_USB0/1
		VDDS3P3V_IOLDO
DCDC5	1.0	CAP_VDD_RTC
DCDC6	1.8	VDDS_RTC
LDO1	1.8	VDDS
		VDDSHVx(1.8 V)
		VDDS_SRAM_CORE_BG
		VDDS_SRAM_MPU_BB
		VDDS_PLL_DDR
		VDDS_PLL_CORE_LCD
		VDDS_OSC
		VDDA1P8V_USB0/1
		VDDA_ADC0/1
		VDDS_PLL_MPU
VDDS_CLKOUT		
LS1	1.2/1.35/1.5 (Tied to DCDC3)	VDDS_DDR

DCDC3 voltage is initially selected through the choice of resistor on the DC34\_SEL pin. Each output voltage can be changed dynamically while the TPS65218D0 is in active mode. This requires use of I<sup>2</sup>C commands to the TPS65218D0.
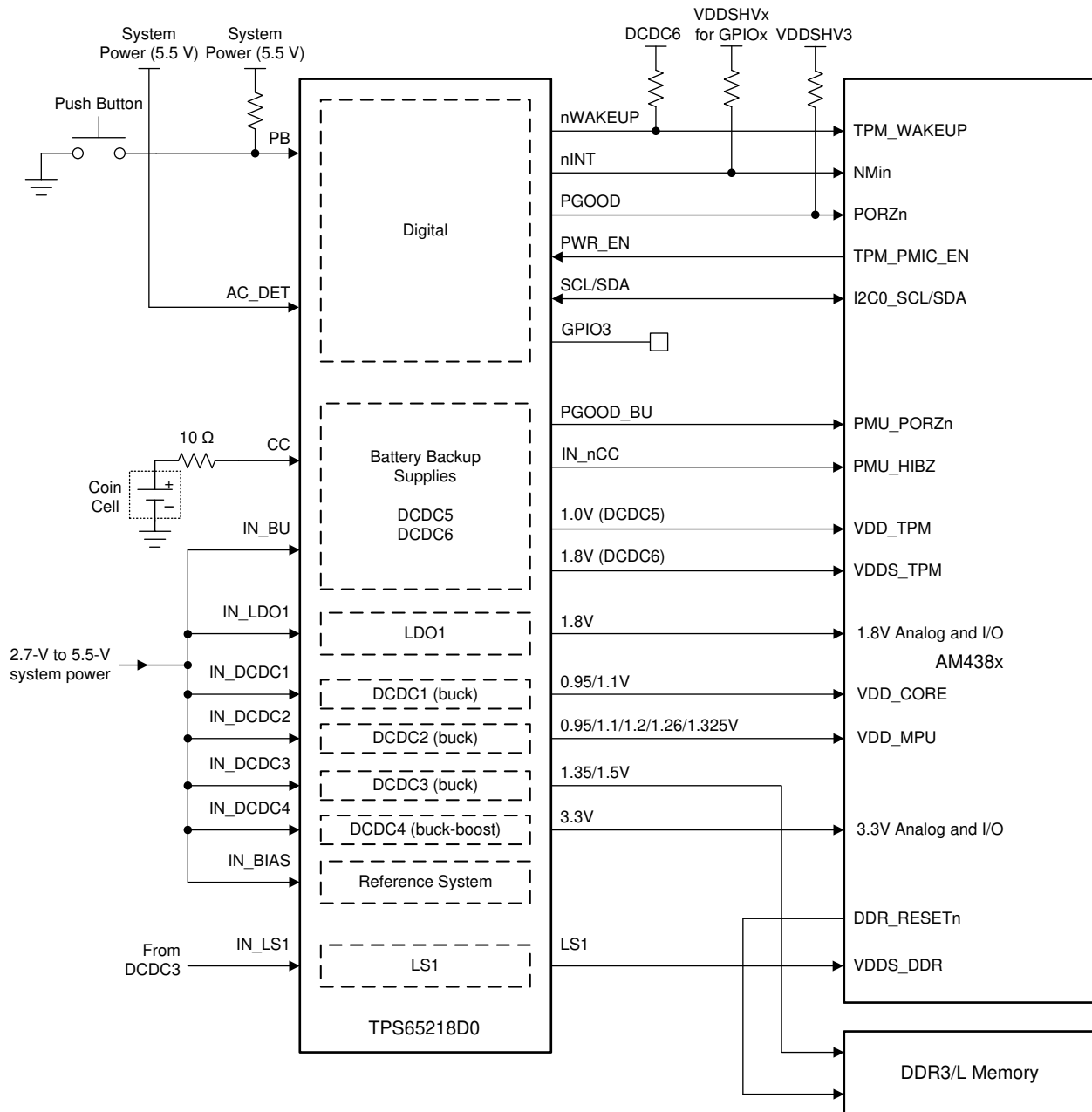
## 6 Connection Diagram for TPS65218D0 and AM438x

The block diagram shown in Figure 3 shows the connections between the TPS65218D0 and AM438x. Power rails and digital and analog signals are shown. The power rails may be used to power additional parts of the system.



Copyright © 2017, Texas Instruments Incorporated

Figure 3. Connection Diagram for TPS65218D0 and AM438x

## 7 Power Rails Connections for TPS65218D0 and AM438x

Table 3 matches the AM438x power terminals with the appropriate power rail from the TPS65218D0.

**Table 3. Power Rails for TPS65218D0 and AM438x**

TPS65218D0D0	Voltage (V)	AM438x
DCDC1	0.95/1.1	VDD_CORE
DCDC2	0.95/1.1/1.2/1.26/1.325	VDD_MPU
DCDC3	1.2/1.35/1.5	LPDDR2/DDR3L/DDR3 Memory
DCDC4	3.3	VDDSHVx(3.3 V)
		VDDA3P3V_USB0/1
		VDDS3P3V_IOLDO
DCDC5	1.0	VDD_TPM
DCDC6	1.8	VDDS_TPM
LDO1	1.8	VDDS
		VDDSHVx(1.8 V)
		VDDS_SRAM_CORE_BG
		VDDS_SRAM_MPU_BB
		VDDS_PLL_DDR
		VDDS_PLL_CORE_LCD
		VDDS_OSC
		VDDA_1P8V_USB0/1
		VDDA_ADC0/1
		VDDS_PLL_MPU
		VDDS_CLKOUT
LS1	1.2/1.35/1.5 (Tied to DCDC3)	VDDS_DDR

DCDC3 voltage is initially selected through the choice of resistor on the DC34\_SEL pin. Each output voltage can be changed dynamically while the TPS65218D0 is in active mode. This requires use of I<sup>2</sup>C commands to the TPS65218D0.

---

**NOTE:** The TPS65218D0 device should be used for AM438x processor.

---

## 8 Power-Up and Power-Down Sequence for TPS65218D0

Figure 4 describes the power-up and power-down sequence of the TPS65218D0. This sequence is specifically optimized for the AM335x, AM437x, and AM438x processor.

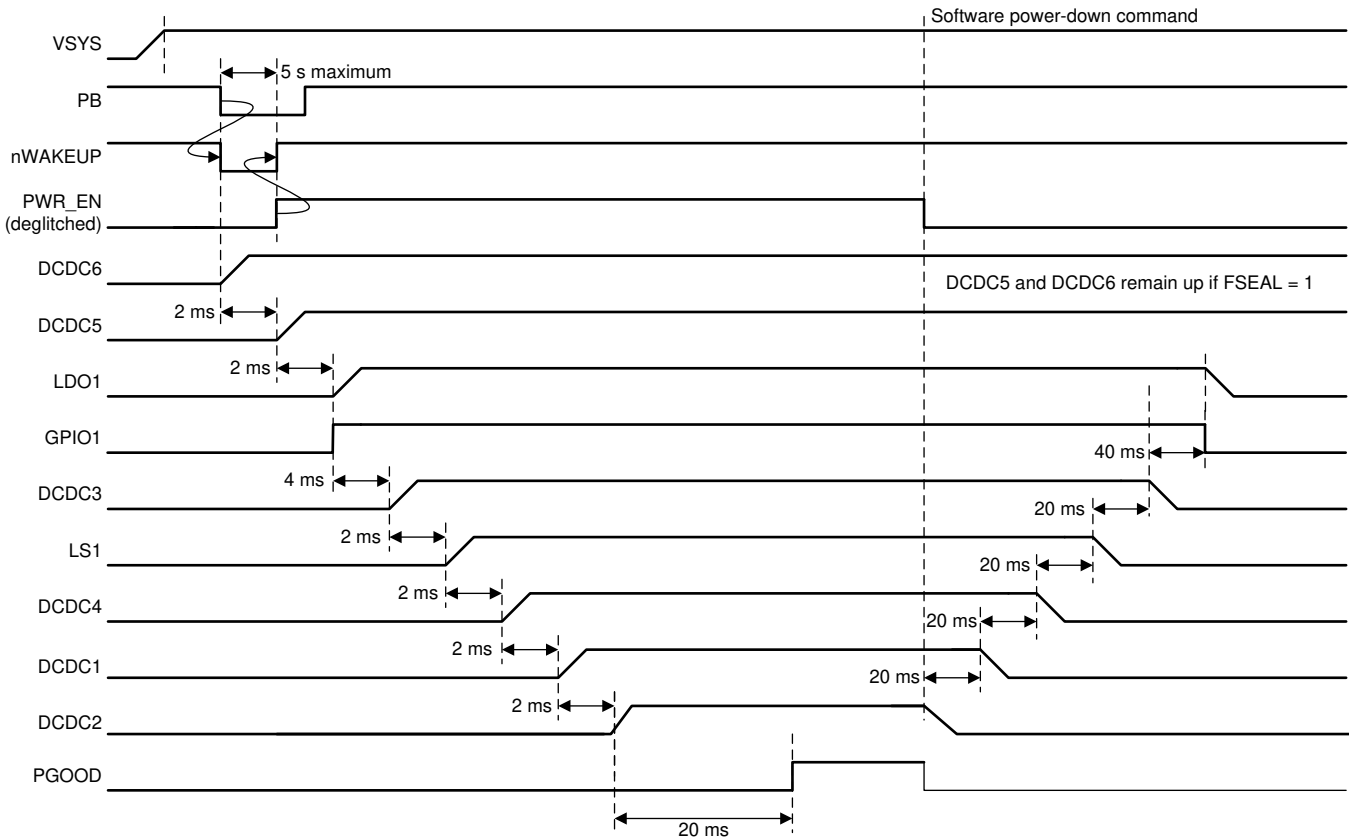


Figure 4. TPS65218D0 Sequence Timing Diagram

The power-up sequence is defined by a series of ten strobes and nine delay times. Each output rail is assigned to a strobe to determine the order in which the rails are enabled. The delay time in-between strobes is 2 ms by default. Table 4 lists the default strobe assignments for TPS65218D0.

Table 4. TPS65218D0 Power-Up Sequence

Strobe 1	DCDC6
Strobe 2	DCDC5
Strobe 3	LDO1
	GPIO1
Strobe 4	
Strobe 5	DCDC3
Strobe 6	
Strobe 7	DCDC4
Strobe 8	DCDC1
Strobe 9	DCDC2
Strobe 10	



## 9 Memory Voltage Selection


DCDC3 can be configured to support a variety of DDR memory voltages. The desired voltage can be selected by placing a 1% resistor to ground on the DC34\_SEL pin. [Table 5](#) lists the available memory voltages and the needed resistor for each.

**Table 5. DCDC3 Voltage Selection**

Memory	DCDC3 Voltage (V)	Resistor (k $\Omega$ )
LPDDR2	1.2	0 (tie to ground)
DDR3L	1.35	12.1
DDR3	1.5	20
DDR2	1.8	31.6

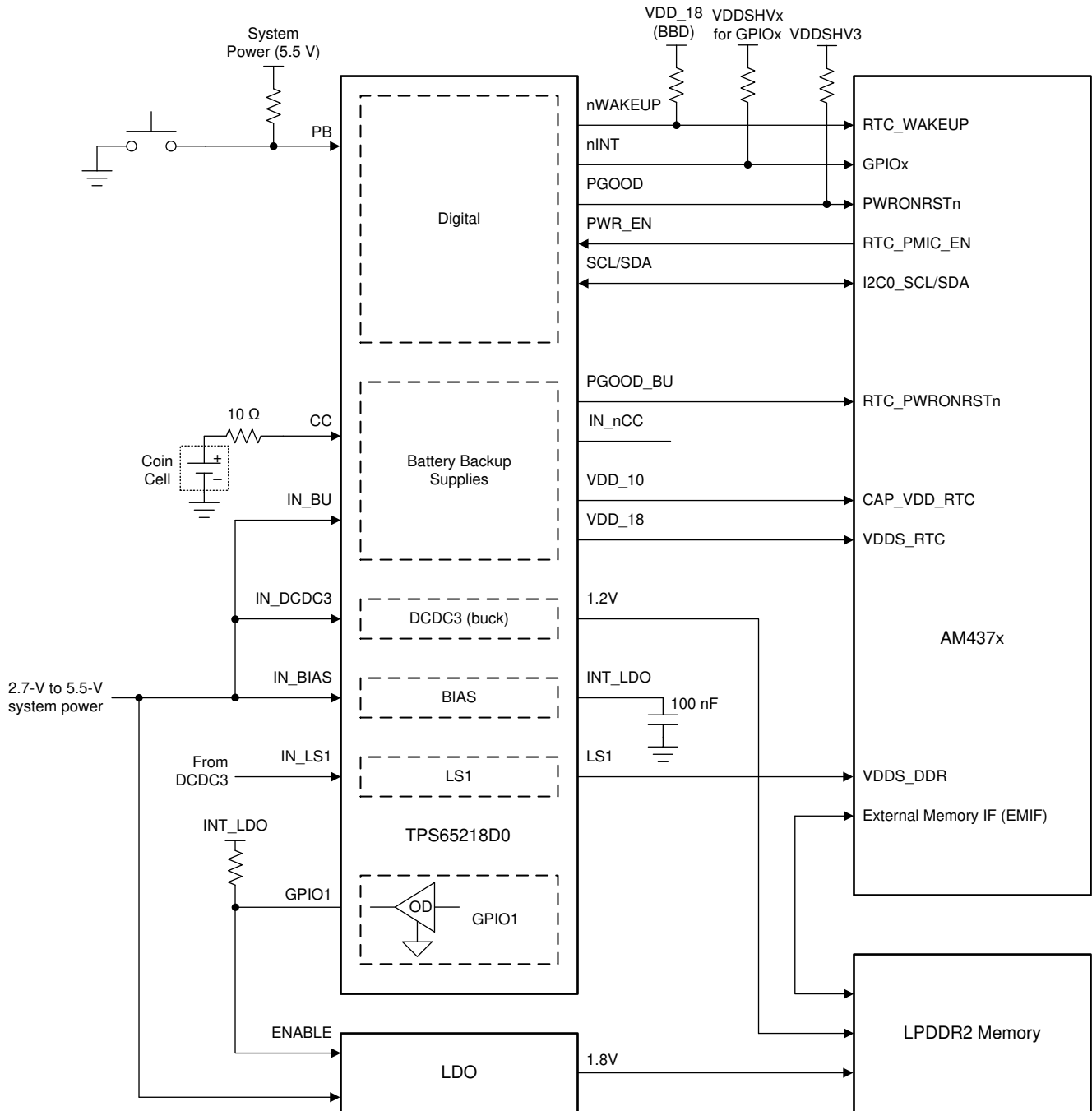
## 10 Using LPDDR2 Memory

If LPDDR2 memory is used, an additional 1.8 V LDO is required. GPIO1 is programmed to properly sequence the additional LDO and should be tied to the LDO enable pin as seen in Figure 5.



Copyright © 2017, Texas Instruments Incorporated

Figure 5. Connection Diagram for TPS65218D0, AM437x, and LPDDR2 Memory

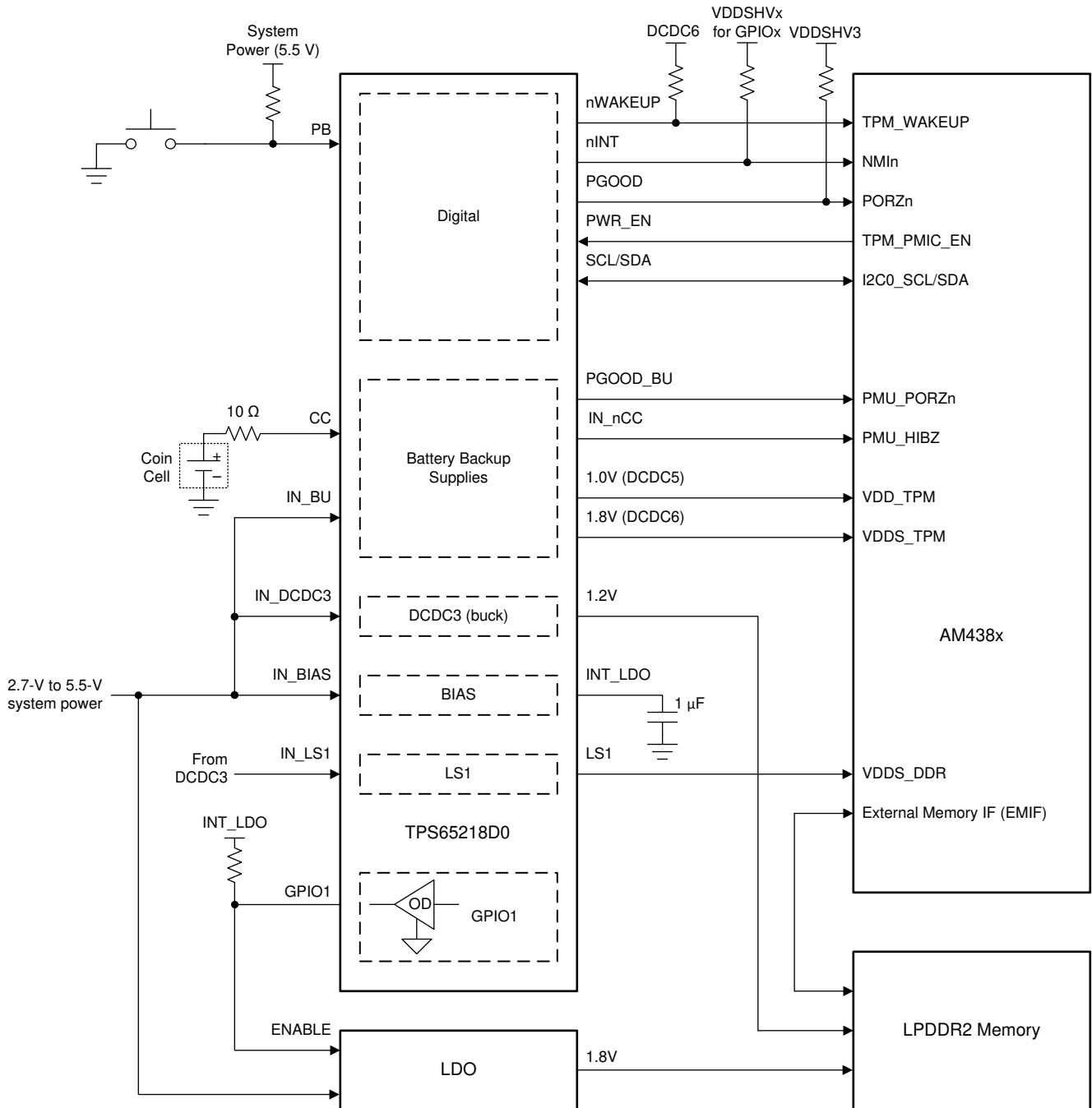


Copyright © 2017, Texas Instruments Incorporated

Figure 6. Connection Diagram for TPS65218D0, AM438x, and LPDDR2 Memory

## 11 Warm Reset

The TPS65218D0 supports warm reset functionality with the AM335x processor. This functionality is enabled on the TPS65218D0 by default, and can be disabled through I<sup>2</sup>C. When enabled, GPIO3 acts as the warm reset input to the PMIC. Asserting GPIO3 low causes DCDC1 and DCDC2 to slew back to their default value of 1.1 V.

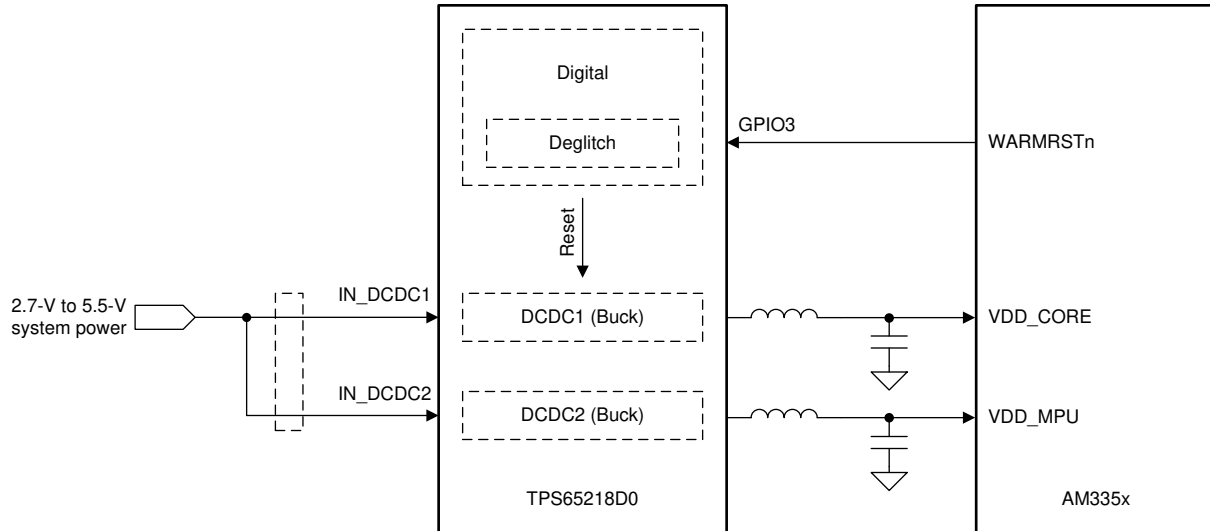

**Figure 7. Warm Reset Functionality**

## 12 Pullup Resistors

There are several pullup resistors needed for operating the TPS65218D0 with the AM335x, AM437x, or AM438x processor. PB should be pulled up to VSYS. nWakeup should be pulled to DCDC6 so that the pullup source is present even during SUSPEND and OFF mode. A 100-k $\Omega$  pullup resistor should be used for nWakeup to minimize the current load on DCDC6. nINT, PGOOD, SCL, and SDA should be pulled up to the same supply that powers VDDSHVx for each signal. SCL and SDA use lower value pullups resistors in order to decrease rise time of these nodes during I<sup>2</sup>C communication.

---

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

---

### Changes from Original (August 2014) to A Revision Page

- Added the *TPS65218D0D0* and *AM438x* Connection Diagram ..... [6](#)
- 

### Changes from A Revision (August 2017) to B Revision Page

- Changed device From: *TPS65218* To: *TPS65218D0* ..... [1](#)
-

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2020, Texas Instruments Incorporated